

## Answer Sheet: Online Examination

Roll No.:	16010121110	
Course	EEE	Page No
Date	25 Feb 12	1

Name of the student:

Satmay Phatre

Signature of the student:

Q.I]

(A) I] If two current sources  $I_A$  ( $7\text{ A}$  and internal resistance of  $6\text{ }\Omega$ ) are connected then equivalent voltage between A & B is

$$(B) V_{AB} = +18V, 3.6 \Omega$$

II] In a Op-Amp based inverting amplifier if feedback gain is 4 and input signal is  $2V$  to peak AC, then output is

(A) 8V peak to peak and in phase with input signal

III] In a Zener diode, if breakdown voltage is high, then

(A) Both P and N are heavily doped

IV] If line voltage of  $450V$  is supplied to  $3\phi$  star type balanced network of pure resistance  $15\Omega/\text{phase}$ , then line current will be

$$(d) 17.32 \text{ A}$$

V] Which DC Motor is most suitable for elevators  
(C) DC series motor

## Answer Sheet: Online Examination

Roll No.:	16010121110	
Course	EEEEE	Page No
Date	25 Feb 22	2

Name of the student:

Satmaj Mhatre

Signature of the student:

Satmaj

(Q1) A)

v<sub>i</sub>] A circuit with resistor inductor and capacitor in series is resonant of  $f_0$ . If all the component values are now doubled, the new resonant frequency is

(C)  $f_0/2$ 

v<sub>ii</sub>] If each branch of a delta network has resistance  $18\Omega$  then each branch of the equivalent star type network has resistance

(B) 6

v<sub>iii</sub>] A parallel resonating circuit consists of Iron core coil of  $R\Omega$  resistance and  $L\text{H}$  inductance in parallel with a capacitor of  $C\text{F}$  behaves like

(B) A pure resistor of value  $R$ .

(x)] In the two wattmeter method of measurement if wattmeter readings are equal and opposite then phase angle of the load is

(b)  $90^\circ$ 

x) The inductive reactance of a  $1\phi$  transformer depends on (D) leakage flux

Roll No.:	16010121110
Course	EEE
Date	25 feb 22 3


Name of the student:

Satmaj Phatre

Signature of the student:

Q1] (B)

(1)

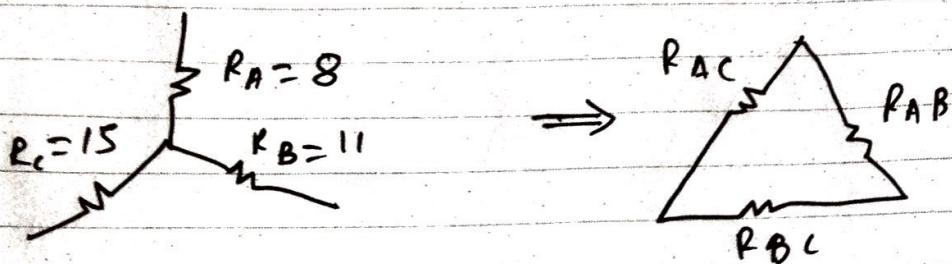

$$R_{AC} = R_A + R_C + \frac{R_A R_C}{R_B}$$

$$= 8 + 15 + \frac{15 \times 8}{11} = 33.90$$


$$R_{AB} = R_A + R_B + \frac{R_A R_B}{R_C}$$

$$= 8 + 11 + \frac{8 \times 11}{15} = 24.867$$

$$R_{BC} = R_B + R_C + \frac{R_B R_C}{R_A}$$

$$= 11 + 15 + \frac{15 \times 11}{8} = 46.625$$

Answer →

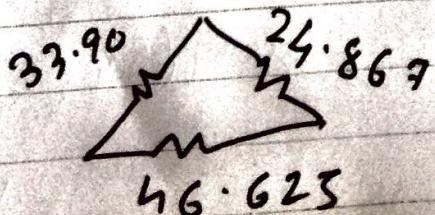


Course	EEE	Page No
Date	23 feb 22	4

Name of the student:


Satmaj Mhatre

Signature of the student:

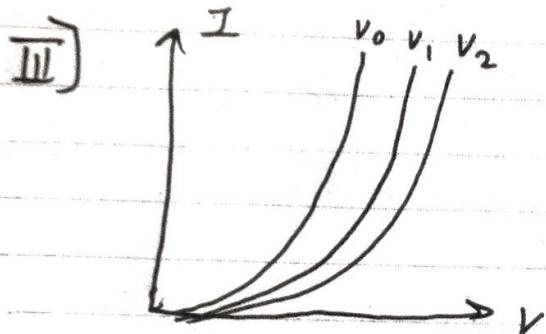Q1) Q2) II]  $I_1 = 20 \sin(\omega t + \pi/4)$   $I_2 = 14 \sin(\omega t - \pi/6)$   
 $\therefore I_1 = 14\sqrt{2} \angle \pi/4$   $I_2 = 7\sqrt{3} \angle -\pi/6$  (convert to phasor)  
 $\therefore I_1 = 10 + j10$   $I_2 = 8.57 + j -4.949$   
 $\therefore I_1 + I_2 = 18.57 + 5.051j = 19.24 \angle 15.21^\circ$   
 $I_N = 24.52 \sin(\omega t + 15.21^\circ)$



Input of CE

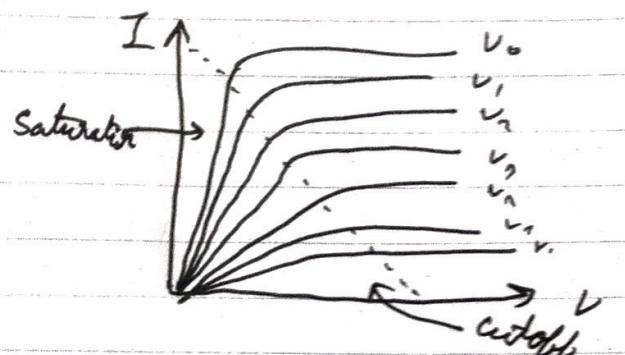

Output of CE

- IV] Advantages of zener diode  $\rightarrow$
- i) Small size can fit in mobile phones
  - ii) Less heat produced
  - iii) Energy efficient
  - iv) Acts as voltage regulator
  - v) Prevents over-voltage and protects devices from damage
  - vi) Low cost alternative

Q1) When two voltage sources are connected in a circuit, each source produces current independent of the other sources and the net resultant current is the vector sum of all independent currents produced. This is called superposition theorem.

## Answer Sheet: Online Examination

Roll No.:	16010121110	
Course	E EEE	Page No
Date	25 feb 22	5

Name of the student:

Satmaj Mhatre

Signature of the student:




(D) (B) vi)

$$V = 15V \quad DC$$

$$I_1 = 16$$

$$I_L = ?$$

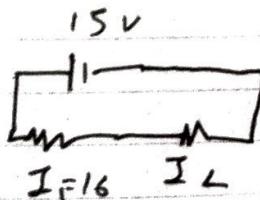

By Maximum power transfer theorem, we know that the maximum power is when  $I_1 = I_L$  and is given by


$$P_{max} = \frac{V^2}{2R} = \frac{15 \times 15}{2 \times 16} = 7.031W$$

Answer → Maximum power absorbed by load resistance is 7.031 W

vii)  $R = 9\Omega$

$$L = 0.12H$$

$$C = 330 \mu F$$

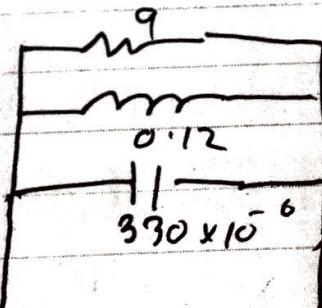

$$Q_F = \frac{\text{Voltage through Capacitor}}{\text{Total Voltage}} = \frac{370}{9} = 36.66$$

## Answer Sheet: Online Examination

Roll No.:	1601012110	
Course	EEEE	Page No
Date	25 feb 22	6


Name of the student:

Aatmaje Mhatre

Signature of the student:

Q2

I

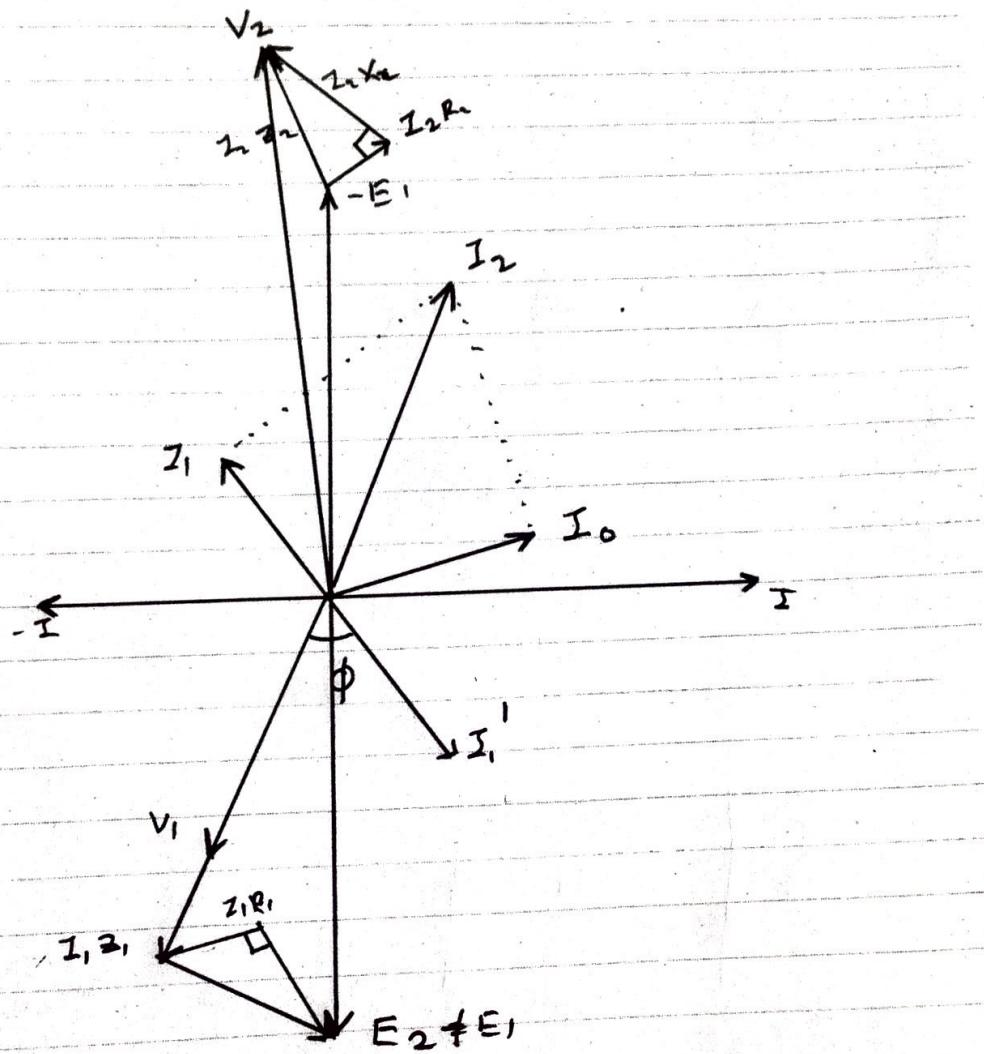

Phasor diagram for single phase transformer considering its winding resistance and magnetic leakages when capacitive load is connected

## Answer Sheet: Online Examination

Roll No.:	1601012110	
Course	EEEE	Page No
Date	25 Feb 22	7

Name of the student:


Satyajit Mhatre

Signature of the student:

(Q2)

$$\text{II] } Z = 15 + j10$$

$$V_s = 400 \text{ V}$$

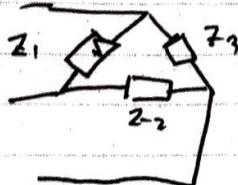

for a delta network,

$$V_L = V_{ph} = 400$$

$$I_{ph} = \frac{V_{ph}}{Z} = \frac{400}{15+j10} = \frac{400}{18.027} \angle -33.69^\circ$$

$$I_L = \sqrt{3} I_{ph} = 22.188 \angle -33.69^\circ$$

$$= 38.432 \angle -33.69^\circ$$

$$W_1 = I_L V_L \cos(30 + \phi)$$

$$W_1 = 15372 \cos(-3.69^\circ)$$

$$W_1 = 15340.13 \text{ Watt}$$

$$W_2 = I_L V_L \cos(30 - \phi)$$

$$W_2 = 15372 \cos(63.69^\circ)$$

$$W_2 = 6813.29 \text{ Watt}$$

Answer

$$W_1 = 15.340 \text{ kW}$$

$$W_2 = 6.813 \text{ kW}$$

## Answer Sheet: Online Examination


Roll No.:	1601012110	
Course	EEE	Page No
Date	25 Feb 22	8

Name of the student:

Aatmaj Mhatre

Signature of the student:

(Q3)

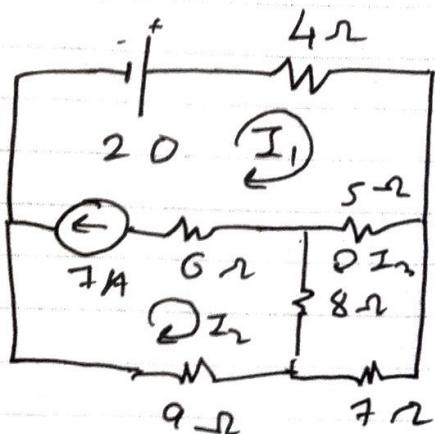

Let  $I_1$  be current in loop 1  
 $I_2$  in loop 2  
 $I_3$  in loop 3

Let direction of  $I_1, I_2, I_3$  be clockwise



In loop 3, apply KVL

$$-5I_3 + 5I_1 - 7I_3 - 8I_3 + 8I_2 = 0$$

$$\therefore 5I_1 + 8I_2 - 20I_3 = 0 \quad \text{--- (1)}$$

In loop 1 & 2, apply supermesh analysis

$$I_1 - I_2 = 7 \quad \text{--- (2) (7 A constant current source)}$$

and

$$-4I_1 - 5I_2 + 5I_3 - 8I_2 + 8I_3 - 9I_2 + 20 = 0$$

$$\therefore -9I_1 - 17I_2 + 13I_3 = -20 \quad \text{--- (3)}$$

## Answer Sheet: Online Examination

Roll No.:	16010121110
Course	EEEE
Date	25 feb 22 9

Name of the student:

Aatmaj Mhatre

Signature of the student:

*Aatmaj*

$$\begin{aligned} \therefore 5I_1 + 8I_2 + -20I_3 &= 0 \\ \therefore 1I_1 + -1I_2 + 0I_3 &= 0.7 \\ \therefore -9I_1 + -17I_2 + 13I_3 &= -20 \end{aligned}$$

$$\therefore \begin{bmatrix} 5 & 8 & -20 \\ 1 & -1 & 0 \\ -9 & -17 & 13 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0.7 \\ -20 \end{bmatrix}$$

$$\begin{aligned} I_1 &= 1.15396 \\ I_2 &= 1.15396 \\ I_3 &= \cancel{1.15396} \end{aligned}$$

$$\begin{aligned} I_1 &= 5.846 \\ I_2 &= -1.153 \\ I_3 &= 1 \end{aligned}$$

$$\begin{aligned} \text{Power absorbed in } 9\Omega &= I^2 R \\ &= (1.153)^2 \times 9 \\ &= 11.964 \end{aligned}$$

(Q4)  $R = 80\Omega, f = 50$


$$V = 240 \text{ V}$$

$$\omega = 2\pi f = 2\pi \times 50 = 314$$

$$I_C = 5$$

$$I_T = 7$$

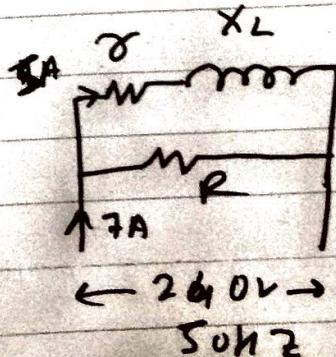To find  $\rightarrow \gamma, \eta, P, X_L$



## Answer Sheet: Online Examination

Roll No.:	16010121110	
Course	EEEE	Page No
Date	25 Feb 22	10

Name of the student:

Satmaj Mhatre

Signature of the student:

Current through pure resistance is

$$I = \frac{V}{R} = \frac{240}{80} = 3 \text{ A}$$

Impedance of the coil is

$$|Z| = \frac{V}{I} = \frac{240}{3} = 48 \Omega$$

$$\text{Total Impedance} = |Z_T| = \frac{V}{I} = \frac{240}{7} = 34.28 \Omega$$

~~From above we know that~~

$$8^2 + 3^2 = 48^2$$

Let current through coil be  $3 \angle A = a + jb$

Let total current be  $7 \angle B = c + jd$

$$\therefore 5 \angle A + 3 \angle 0 = 7 \angle B \quad (\text{vector sum})$$

$$\therefore a + jb + 3 + 0j = c + jd$$

$$\begin{aligned} \therefore a + 3 &= c \\ b &= d \end{aligned}$$

But we know  $a^2 + b^2 = 5^2$   
 $c^2 + d^2 = 7^2$

Roll No.:	16016121110	
Course	EEEEE	Page No
Date	25 feb 22	91

Name of the student:

Aatmaj Nhatre

Signature of the student:



Now we have

$$\begin{aligned} a^2 + b^2 &= 5^2 \\ (a+3)^2 + b^2 &= 7^2 \end{aligned}$$

$$\therefore a^2 + b^2 + 6a + 9 = 7^2$$

$$\therefore a^2 + b^2 + 6a + 9 = 49$$

$$\therefore 25 + 6a = 40$$

$$\therefore 6a = 15$$

$$\therefore a = 2.5$$

$$\therefore b = \pm 4.33$$

$$\therefore c = 5.5$$

$$d = 5.33$$

$$\therefore \tan^{-1}\left(\pm \frac{b}{a}\right) = \pm 60^\circ$$

$$B = \tan^{-1}\left(\frac{d}{c}\right) = \pm 38.21^\circ$$

$$\therefore \phi = B = 38.21^\circ$$

$$\text{Power factor} = \cos \phi = \cos 38.21^\circ = 0.7857$$

$$\text{Power} = V \times I \cdot \cos \phi$$

$$= 7 \times 240 \times 0.7857 = 1320.058 \text{ W}$$

## Answer Sheet: Online Examination

Roll No.:	16010121110	
Course	EEE	Page No.
Date	25 Feb 22	12

Name of the student:

Satmay Phatre

Signature of the student:

*Satmay*

~~Power~~ for coil,  $\phi = A - 60^\circ$  (consider  $\phi = -60$  and not  $\phi = +60$ )

$\therefore$  Power factor -  $\cos(\phi) = \cos 60^\circ = 0.5$

$$\begin{aligned}\therefore \text{Power absorbed by coil} &= VI \cdot \cos \phi \\ &= 240 \times 5 \times 0.5 \\ &\approx 600 \text{ W.}\end{aligned}$$

Current through coil = ~~is~~  $5 L-60$

$$Z = \frac{V}{I} = \frac{240}{5 L-60} = 48 L+60$$

$$\therefore Z = 24 + 41.57i$$

$$\therefore r = 24$$

$$X_L = 41.57$$

$$\therefore wL = 41.57$$

$$\therefore L = \frac{41.57}{314} = 0.132$$

$$\text{Answer} \rightarrow L = 0.132 \text{ H}$$

$$r = 24 \Omega$$

$$P_{\text{coil}} = 600 \text{ W}$$

$$P_{\text{tot}} = 1320 \text{ W}$$

## Answer Sheet: Online Examination

Roll No.:	16010121110	
Course	EEE	Page No
Date	25 feb 22	13

Name of the student:


Satmaje Mhatre

Signature of the student:

*Satmaje*

(Q2)


III

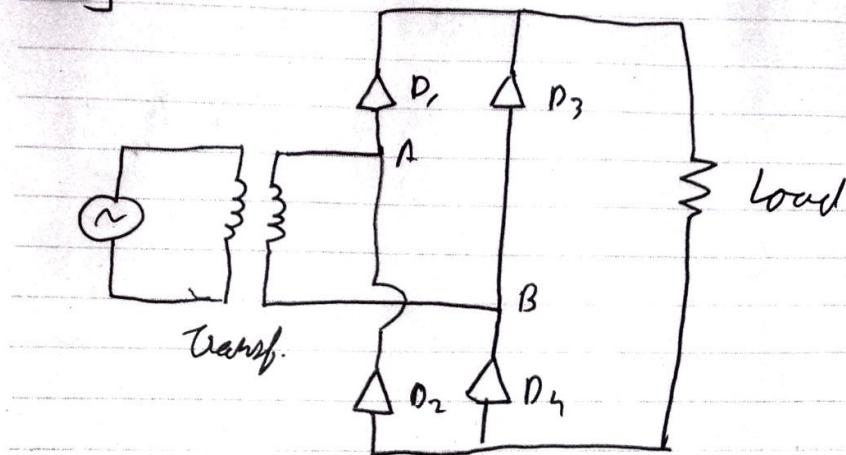

Single phase  
bridge rectifier

D, D<sub>2</sub> D<sub>3</sub> D<sub>4</sub> → Diodes

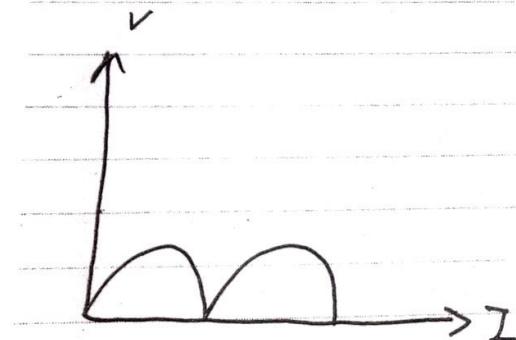Both cycles are utilized  
by this type of  
transformer



output

When current is in +ve cycle, it passes through A - D<sub>1</sub> - D<sub>4</sub> - B

When current is in -ve cycle it passes through

B - D<sub>3</sub> - D<sub>2</sub> - A

So load experiences only linear current throughout both cycles.

## Answer Sheet: Online Examination

Roll No.:	16010121110	
Course	EEEEE	Page No
Date	25 Feb 22	15

Name of the student:




Aatmaj Mhatre

Signature of the student:

*Aatmaj*

(Q3) Norton →

$$Req =$$

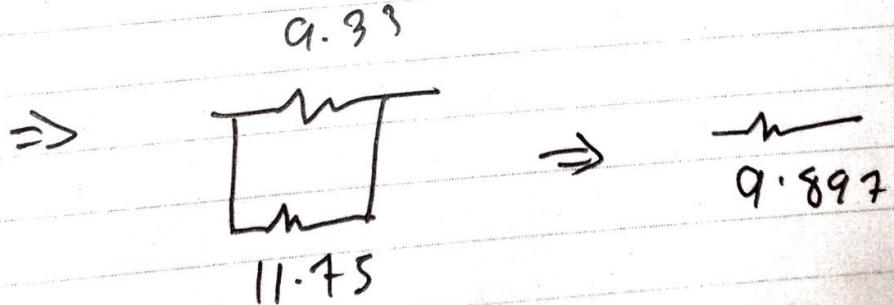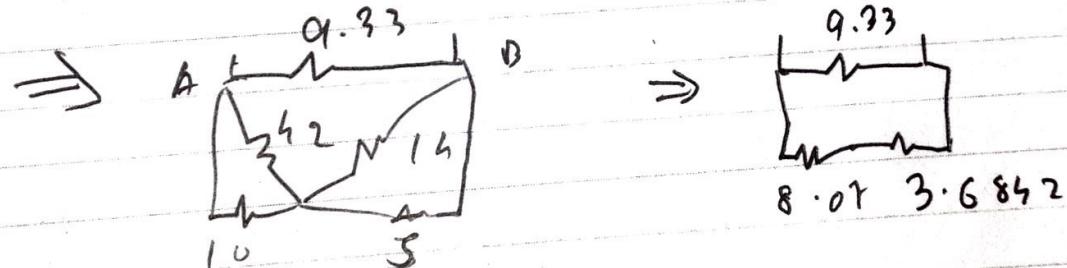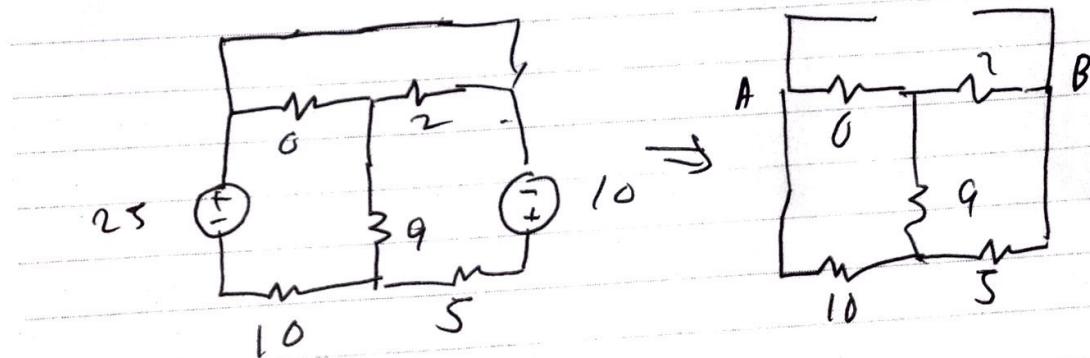

$$\therefore Req = 9.897$$